



You should add ports, wires, and MUXs to complete the diagram